

COL215 Hardware Assignment 2

~by Adithya Bijoy and Anish Banerjee

(2021CS10571 and 2021CS10134)


Design Decisions and Lab Work

We added the decimal point in our timing module and used the combine module created in the last assignment. We made two counters, counter1 for incrementing after each clock period (10ns) and counter2 for incrementing whenever counter1 reaches 10^7 . Counter2 represents the count for 10^{th} second. Using counter2, we derive the values of minutes, tens of seconds, unit of seconds and tenths of seconds.


Then we made the logic for enable_watch and reset_watch using their truth tables, and controlled the counters using these two signals.

Simulations

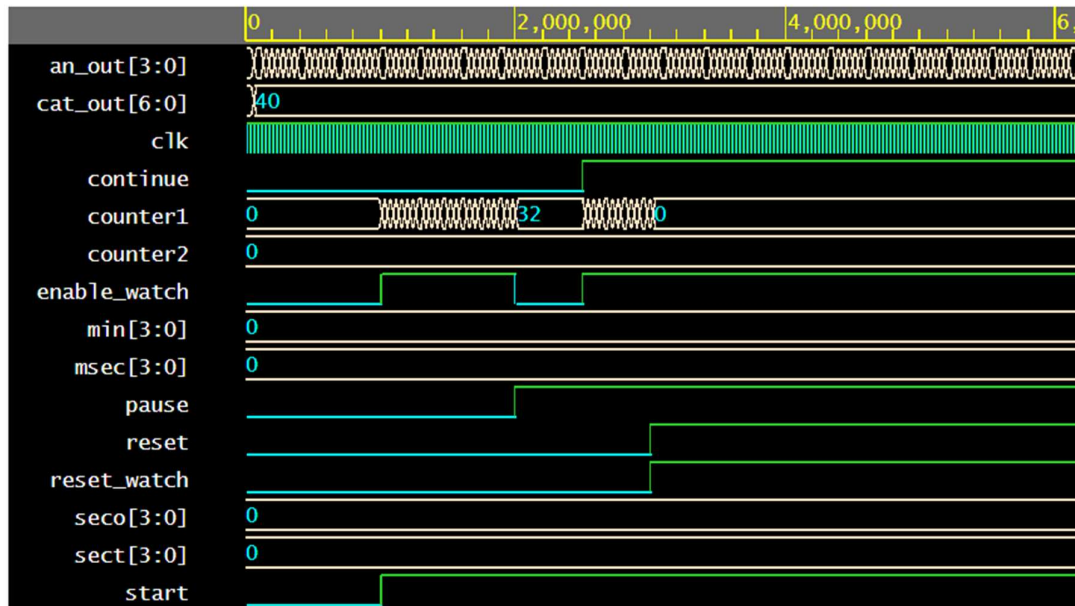Showing working of start, pause, reset and continue



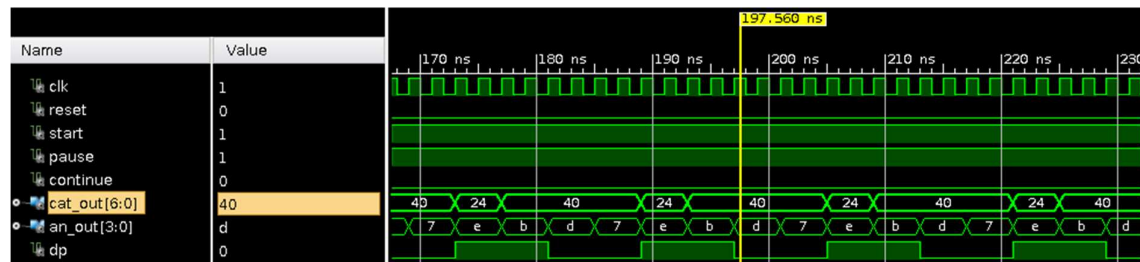On pressing pause, the display gets stopped



On continue, it starts again

