



Digital Logic and System Design

8. Registers, Counters, and Memory

COL215, I Semester 2022-2023

Venue: LHC 111

'E' Slot: Tue, Wed, Fri 10:00-11:00

Instructor: Preeti Ranjan Panda



panda@cse.iitd.ac.in

www.cse.iitd.ac.in/~panda/

Dept. of Computer Science & Engg., IIT Delhi


Registers

 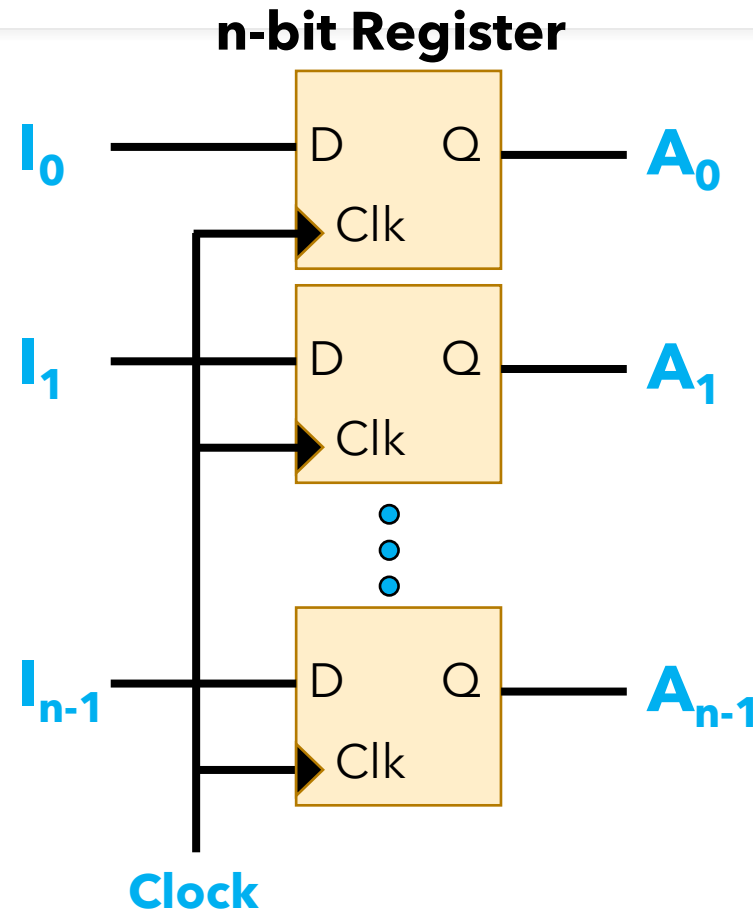- Group of Flip-flops
 - common **clock**
 - stores **1 bit** per flip-flop
- Recall: **State Register** of FSM
- n-bit value transferred from Ds to Qs on clock edge
 - storing **n-bit data**




Registers with Reset

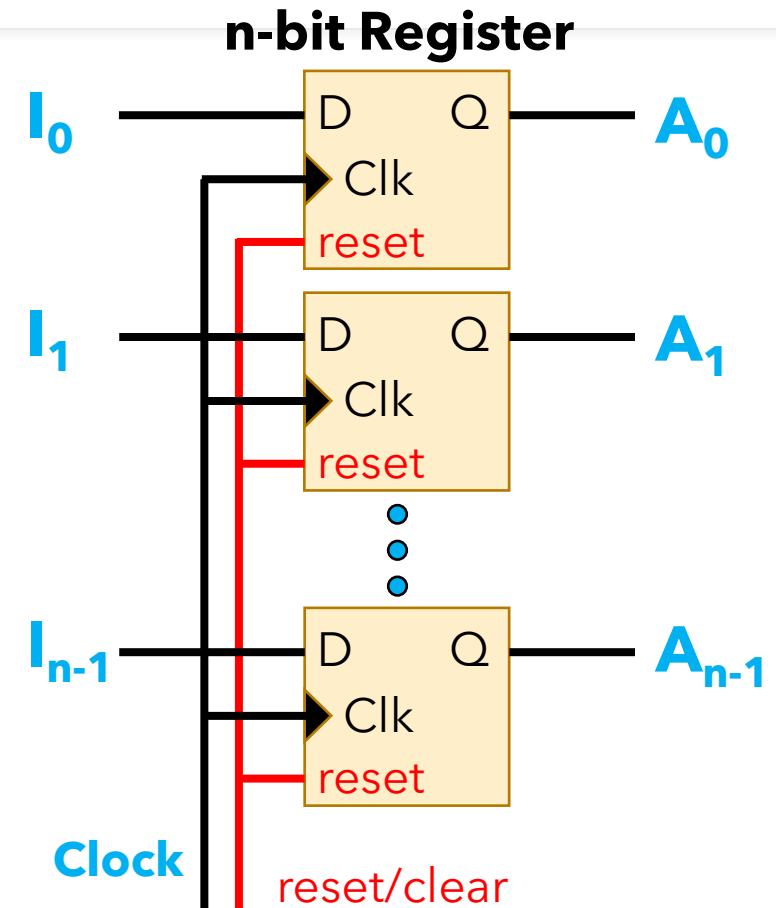- **Reset/Clear** signal **asynchronously** clears **A** to **0**
 - independent of Clk
 - using DFF with asynchronous Reset





Registers with **Load** signal

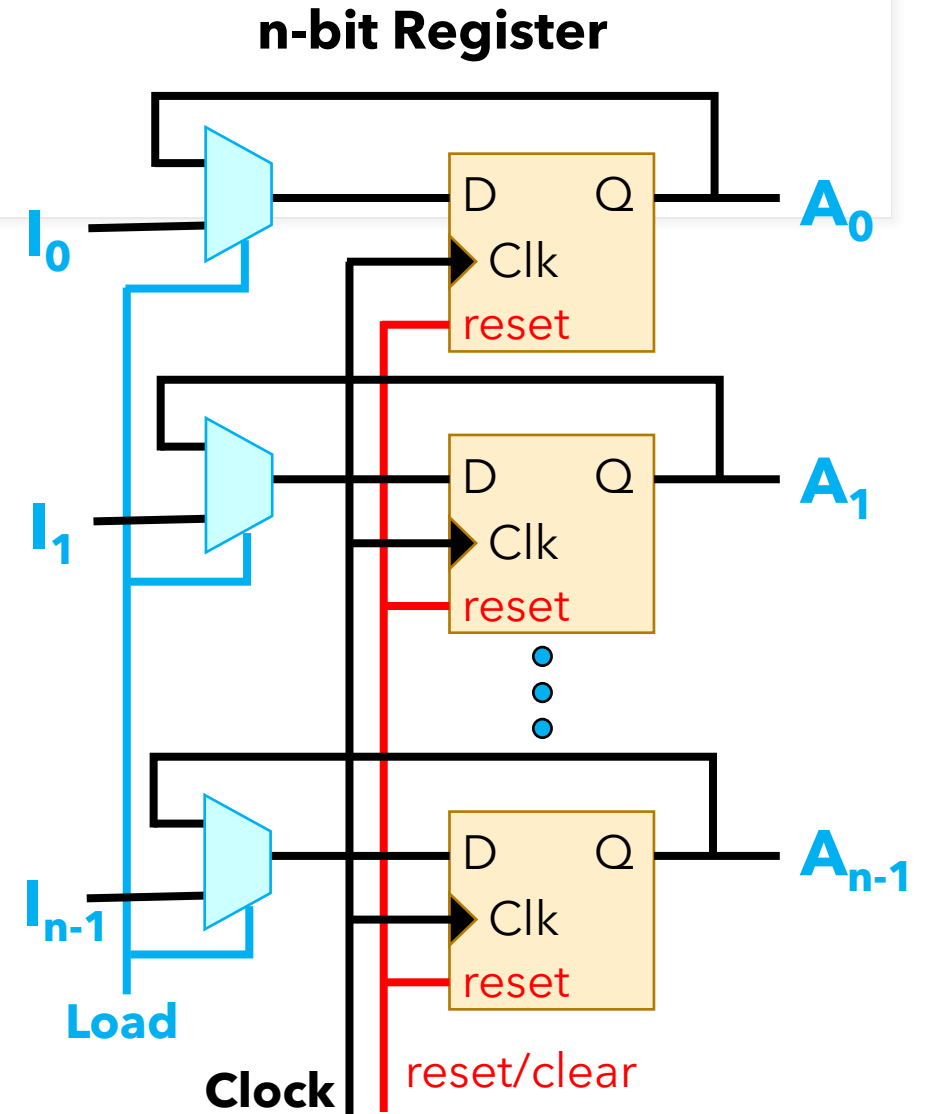- Register function:
 - Transfers I to A on every clock
 - Called **Loading** new value to register (or **updating** the register)
- Desired function:
 - Load new value **only when required**
 - New control signal **Load**
- **Modify D input**
 - **Not clock** (don't disturb clock, causes uneven propagation delays)



Shift Registers

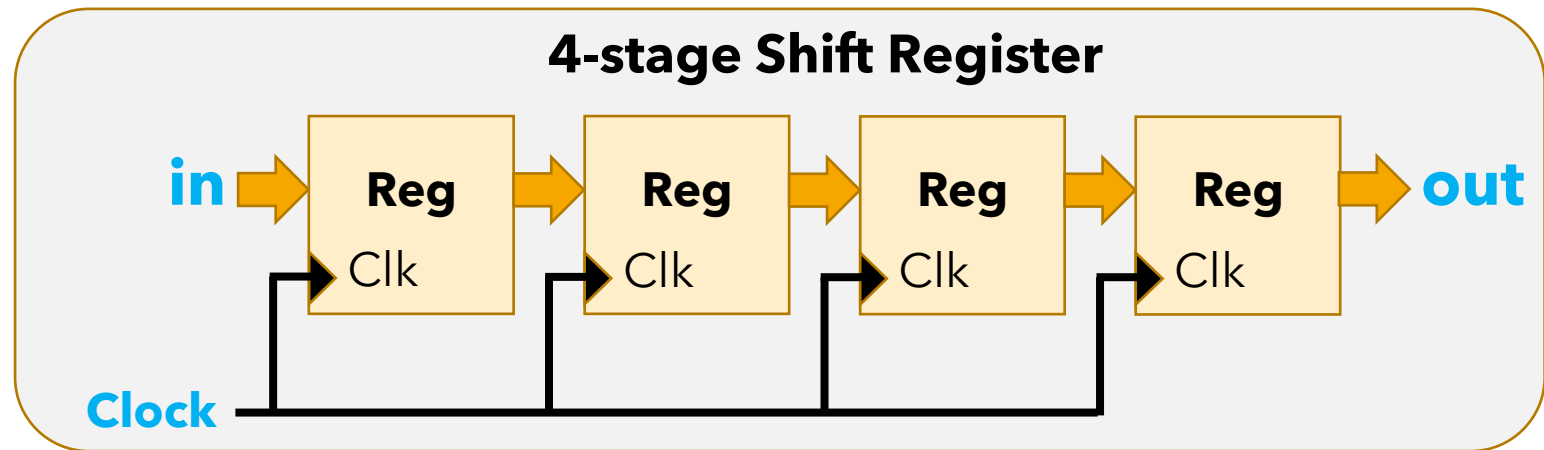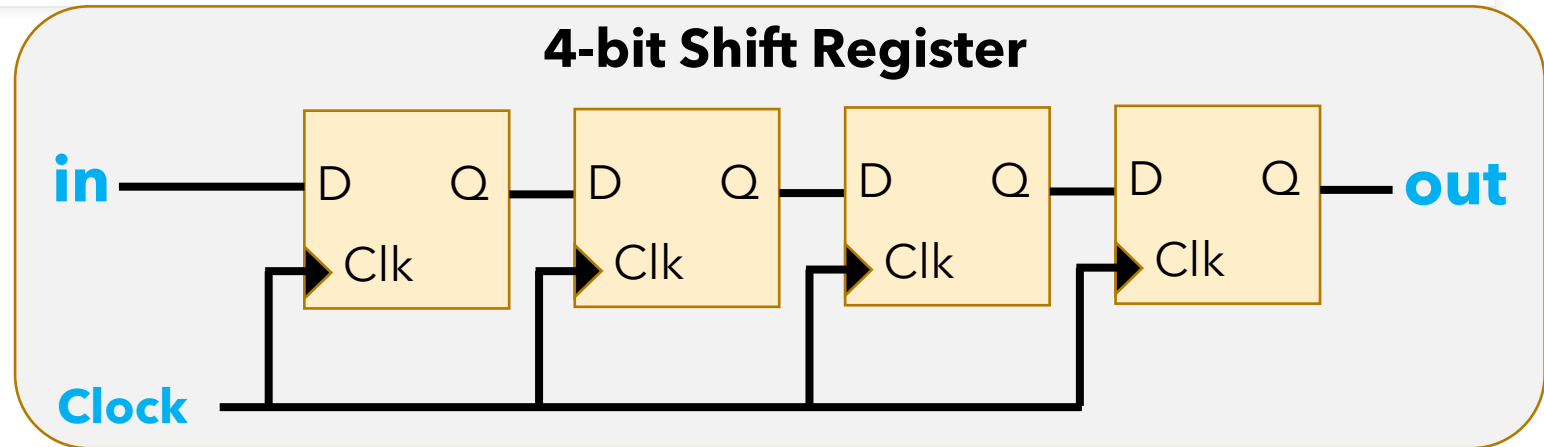- **Cascade/Chain:** Q of one stage connected to D of next stage
- Common **Clock**
- **Shifts** bit to next DFF on clock edge
- General: Chained **data registers** (n-bits wide)



Counters

- Register going through a given **sequence of states on input pulse**
- Already studied: **mod 3 counter**
 - Sequence: 0,1,2,0,1,2,0,1,2
- Counting on common **clock pulse**:
synchronous counter (e.g., mod 3 counter)
- Pulse could be internal signal: **ripple counter**
- Counter value on **Q of DFFs**

B ₂	B ₁	B ₀	Sequence ↓
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Counters

- How do we generate sequence for DFF **B₀**?
 - Alternating Sequence
- How do we generate sequence for DFF **B₁**?
 - Alternating Sequence
 - Triggered by?
- How do we generate sequence for DFF **B₂**?
 - Alternating Sequence
 - Triggered by?

DFF: B₂ B₁ B₀

0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Sequence

Counters

- How do we generate sequence for DFF **B₀**?
 - Alternating Sequence
 - Triggered by **External Count Signal**
- How do we generate sequence for DFF **B₁**?
 - Alternating Sequence
 - Triggered by **Negative edge of B₀**
- How do we generate sequence for DFF **B₂**?
 - Alternating Sequence
 - Triggered by **Negative edge of B₁**

DFF: B₂ B₁ B₀

0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


Sequence

Ripple Counters



DFF:

B_2	B_1	B_0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


Sequence

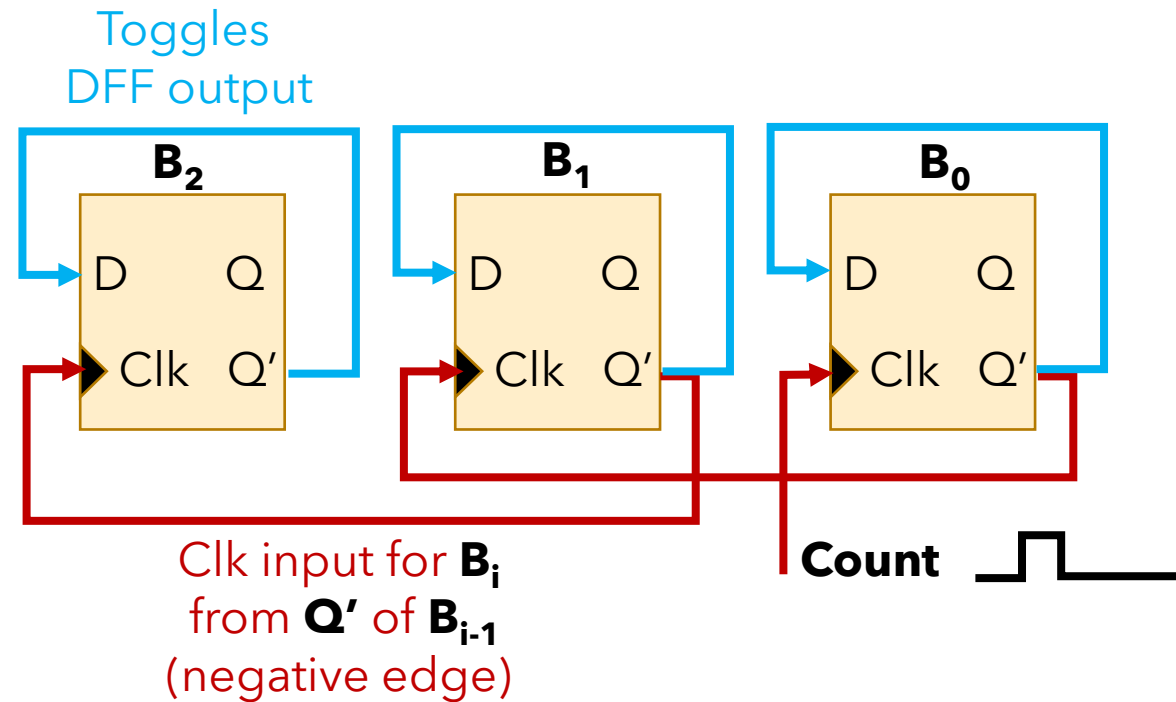


Recall: Memory Interface and Function

 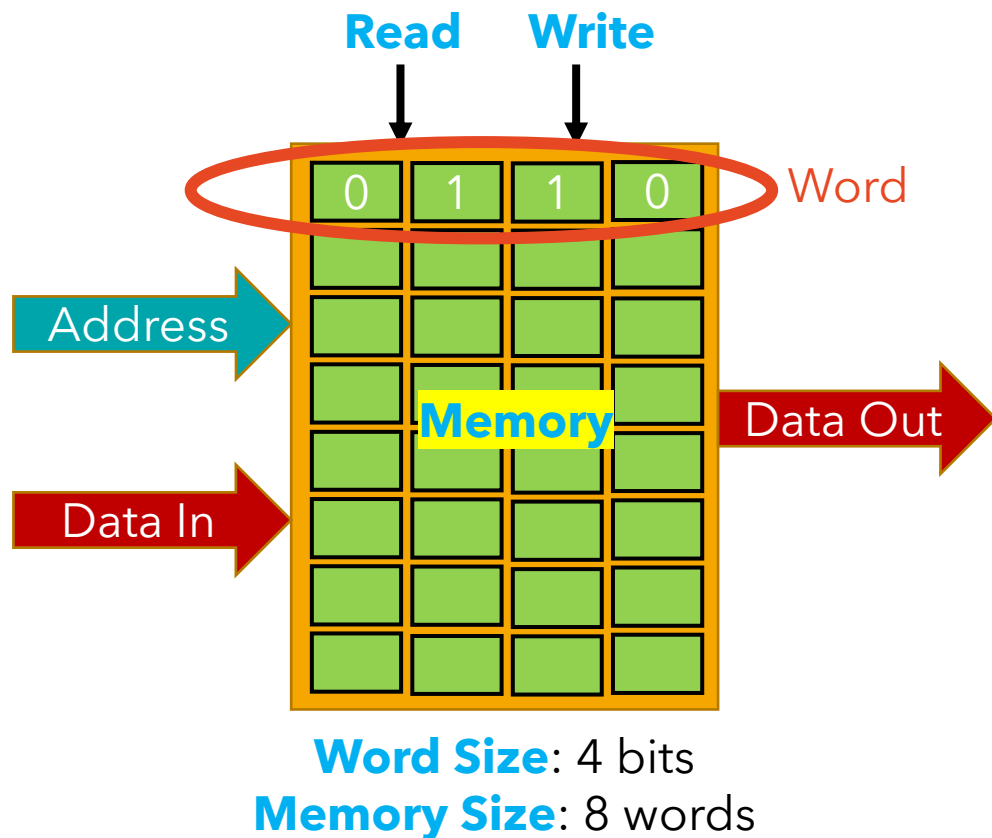

Memory Cell

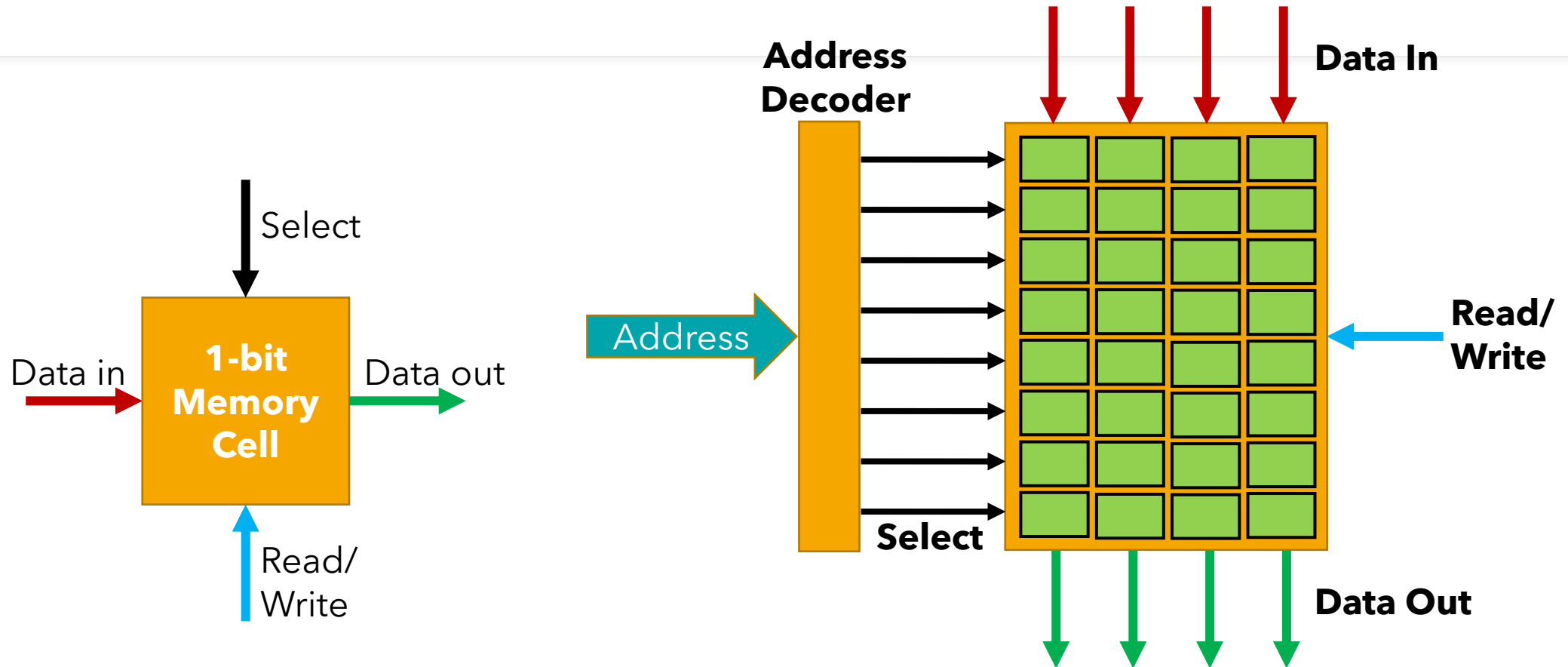


Recall: Decoder Implementation

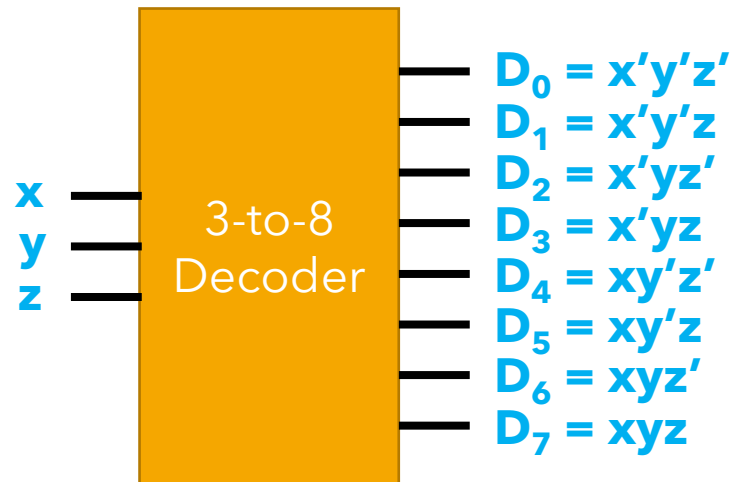


Each output is a **minterm**

Truth Table?


a	b	c	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 


Memory Cell and Array

 

Memory Cell

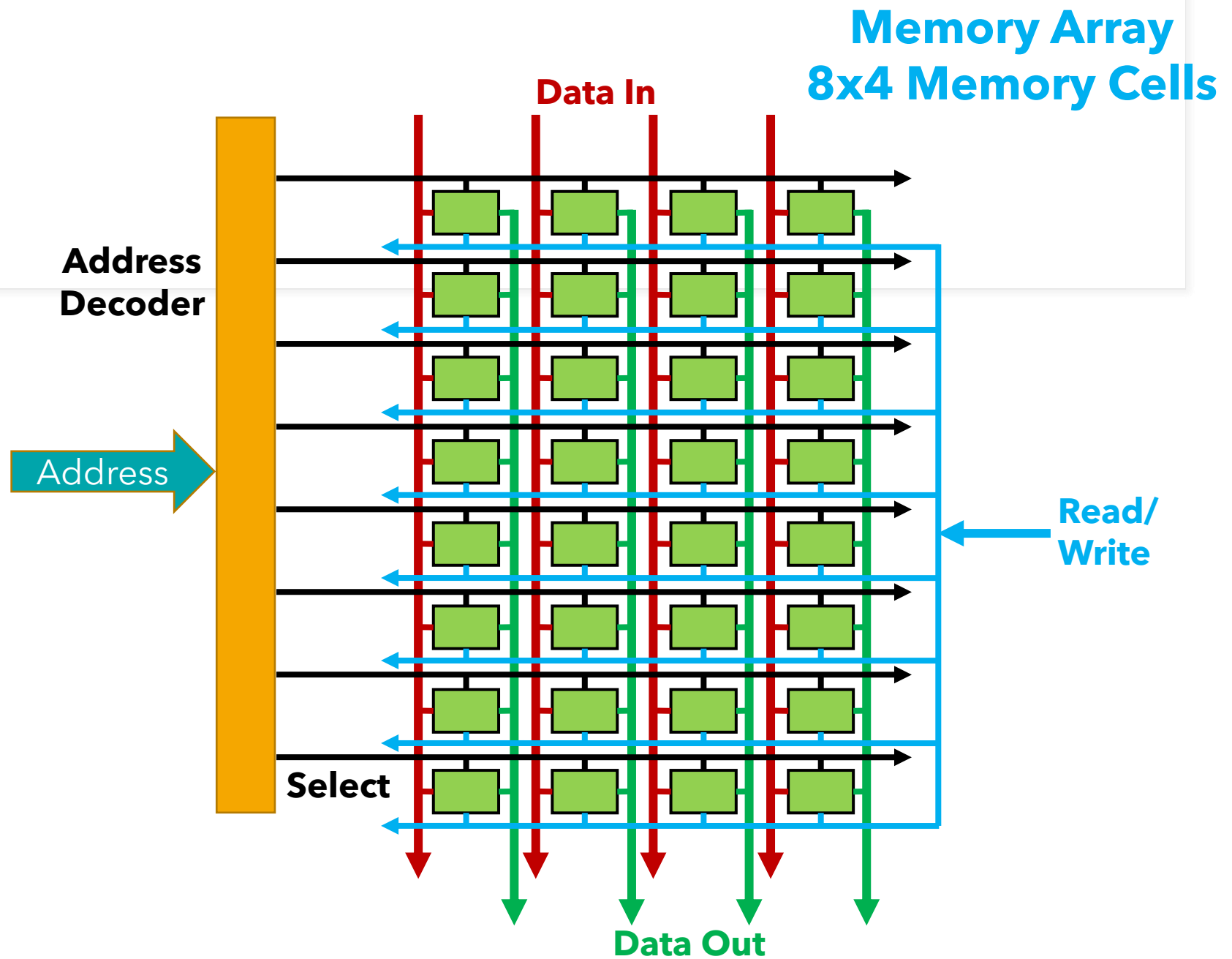


2D Memory Layout

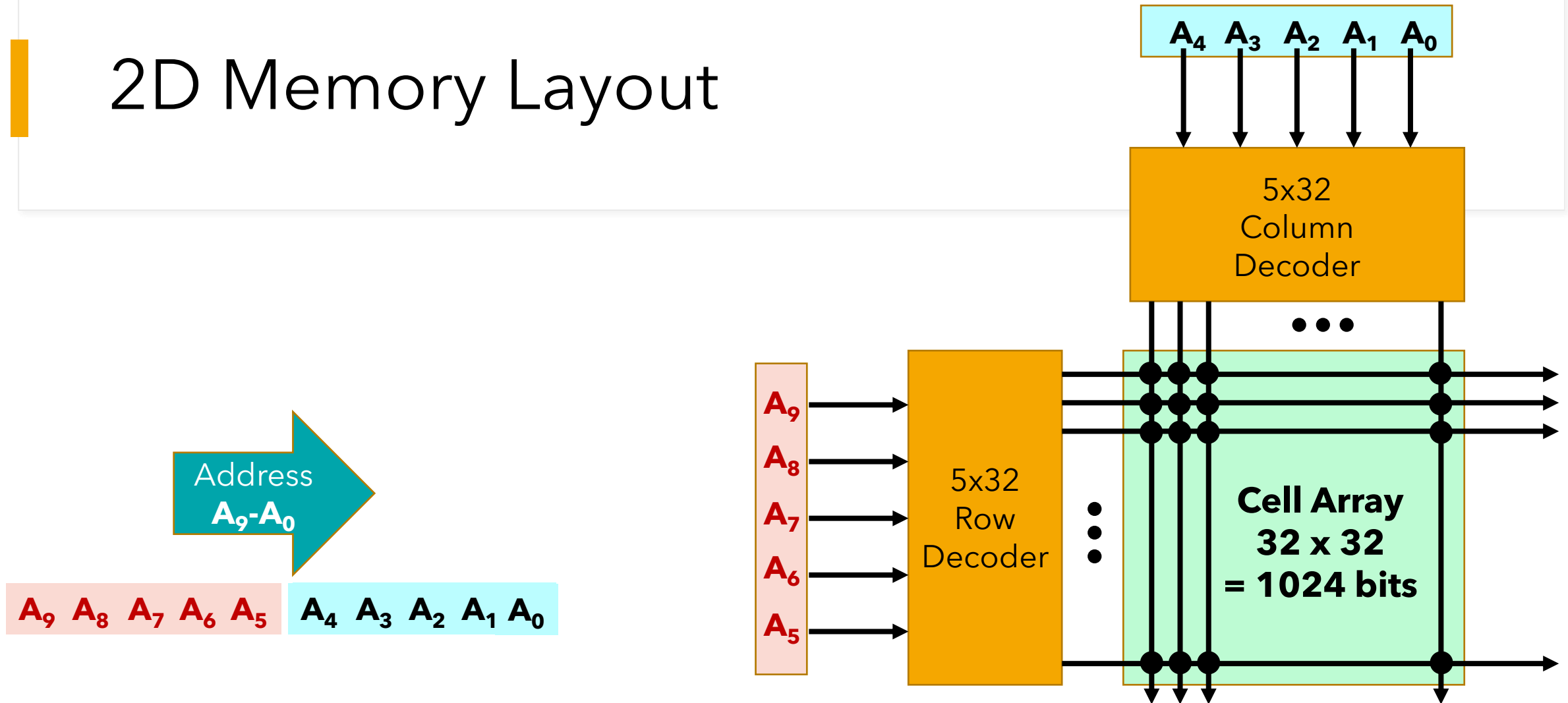


Data Arranged in Square/Rectangle

DRAM Addressing

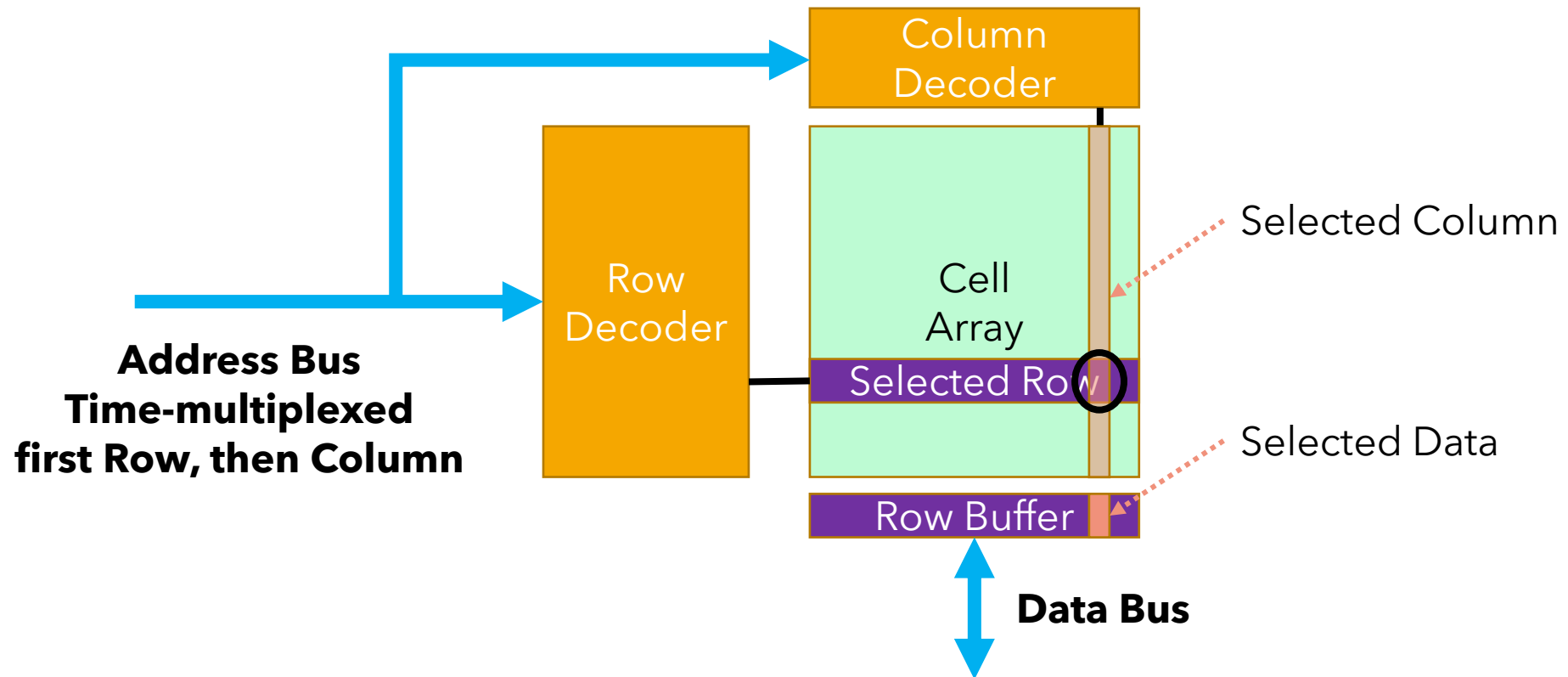

DRAM Addressing

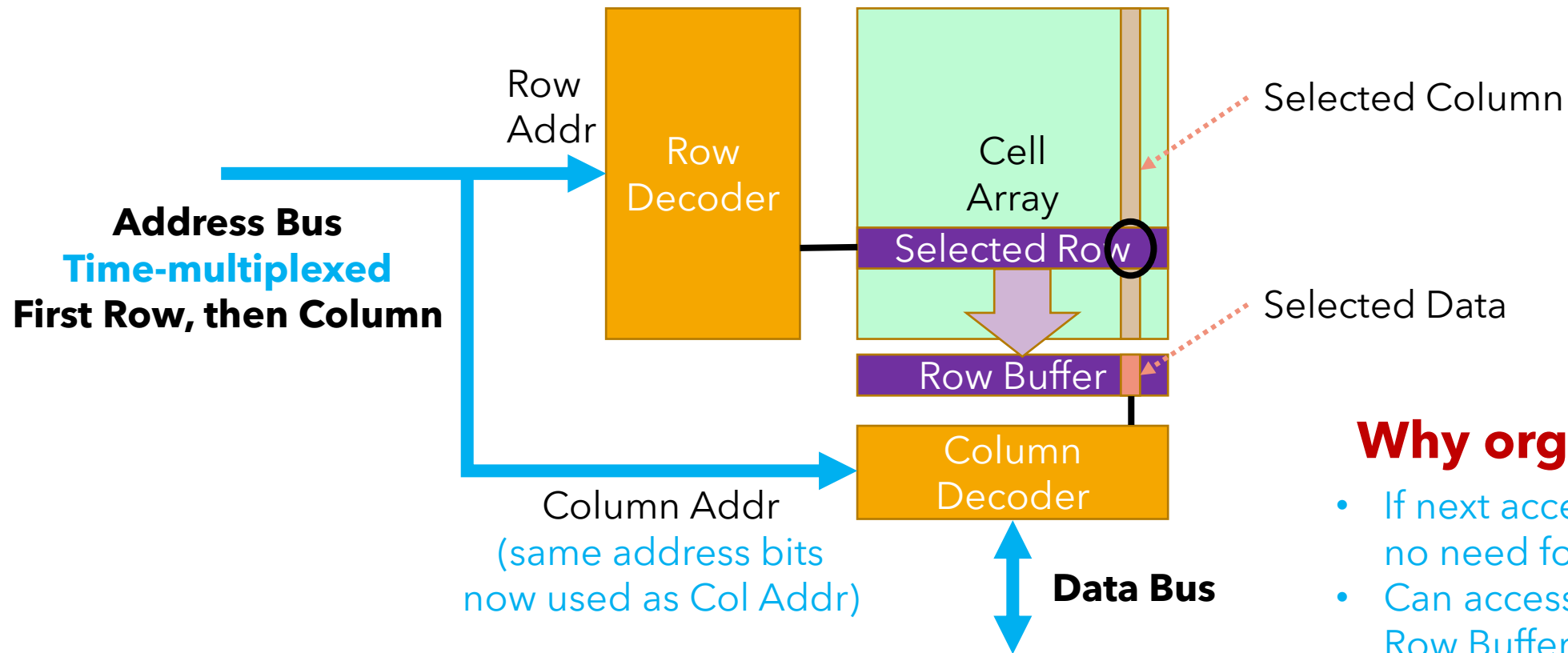


Why organize this way?


- If next access is to same row, no need for Row Decoding
- Can access data directly from Row Buffer. Only Col Decoding

Error Detection


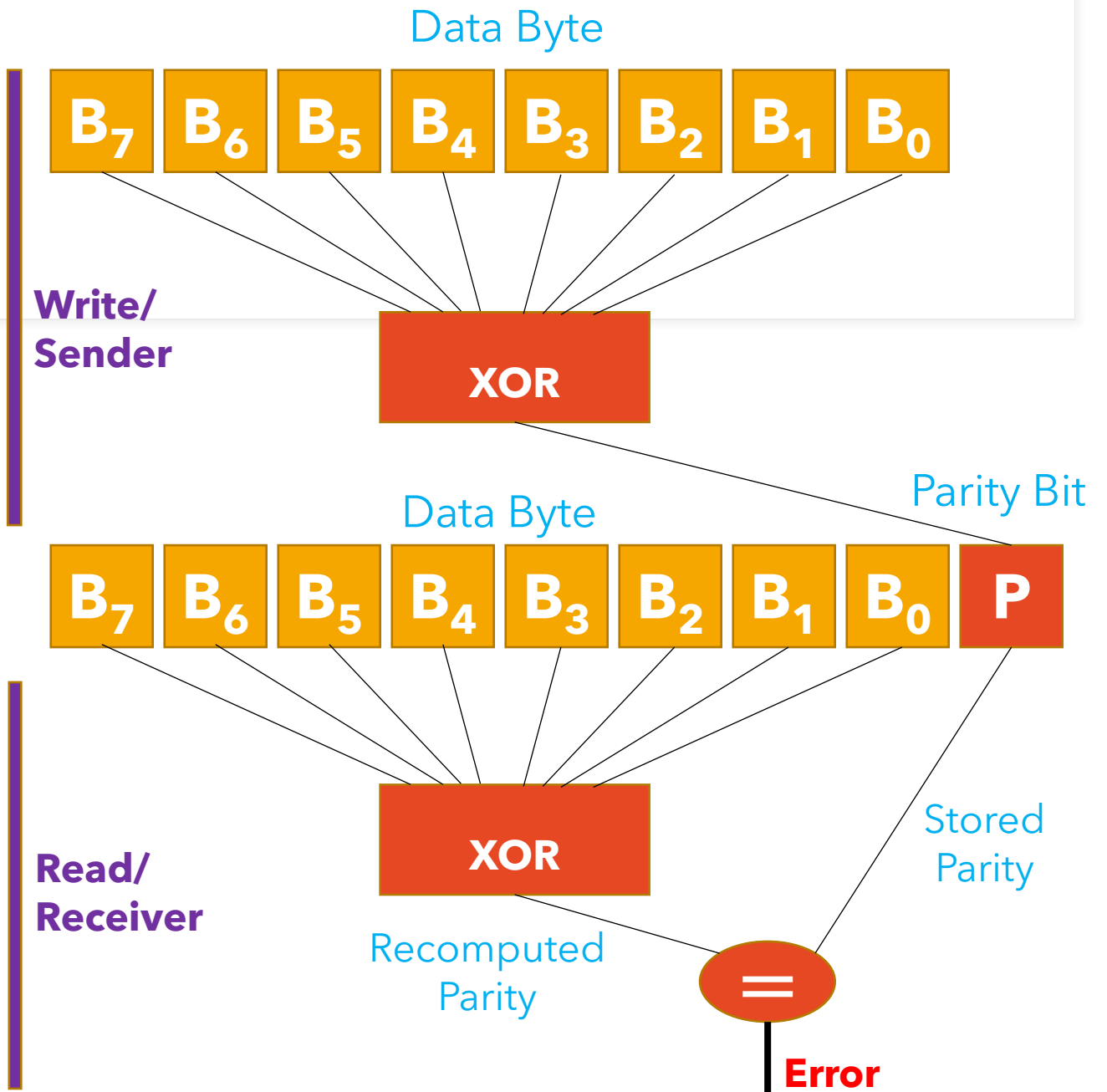
- Errors might occur in storage and transmission
- Error Detection: **Parity Bit**
- Parity: Additional bit stored along with data
- Parity **re-computed** by receiver, **compared** with stored parity
- If different, **error**



Error Correction with Hamming Codes

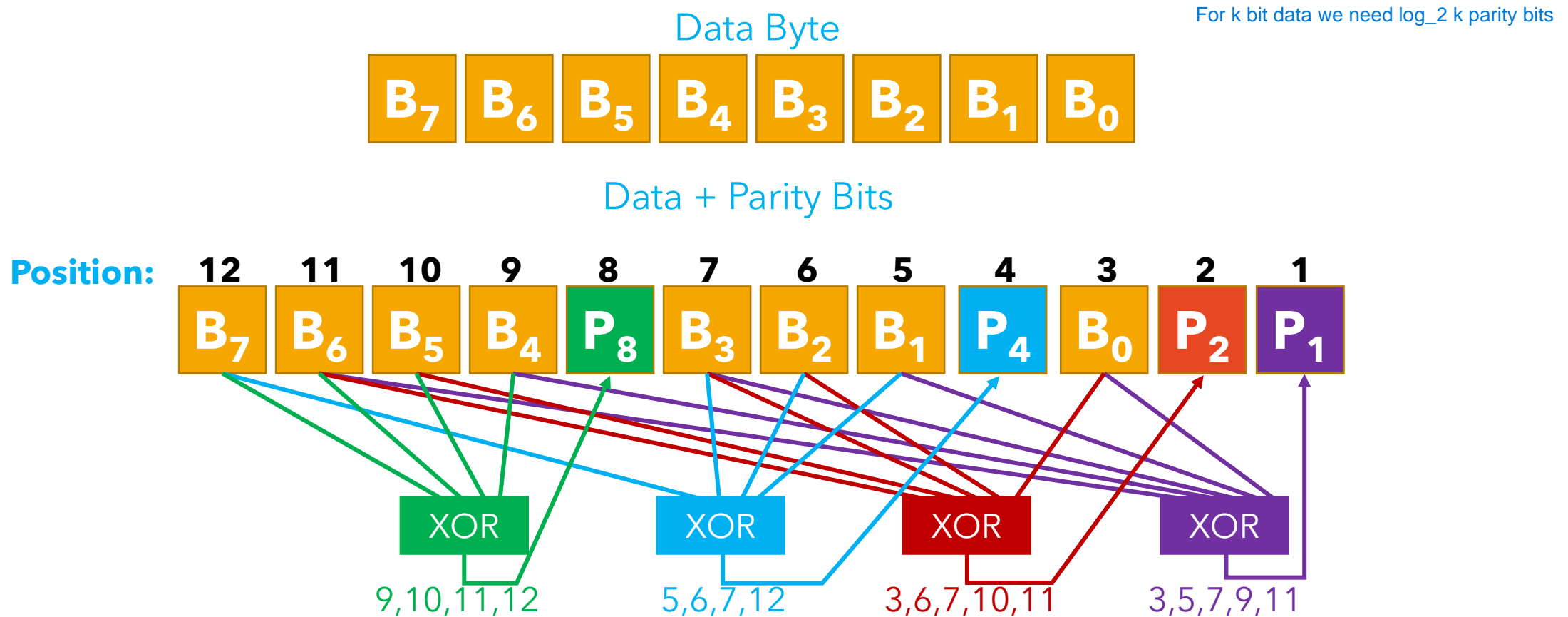

Error Correction with Hamming Codes

  



C₁ = ?

0 if bits 1,3,5,7,9,11 **OK**

1 if **error** on any of bits 1,3,5,7,9,11

Including Parity Bit
Error type: single bit flip


Error Correction with Hamming Codes

  

C₂ = ?

0 if bits 2,3,6,7,10,11 OK
1 if **error** on any of bits 2,3,6,7,10,11

Error Correction with Hamming Codes

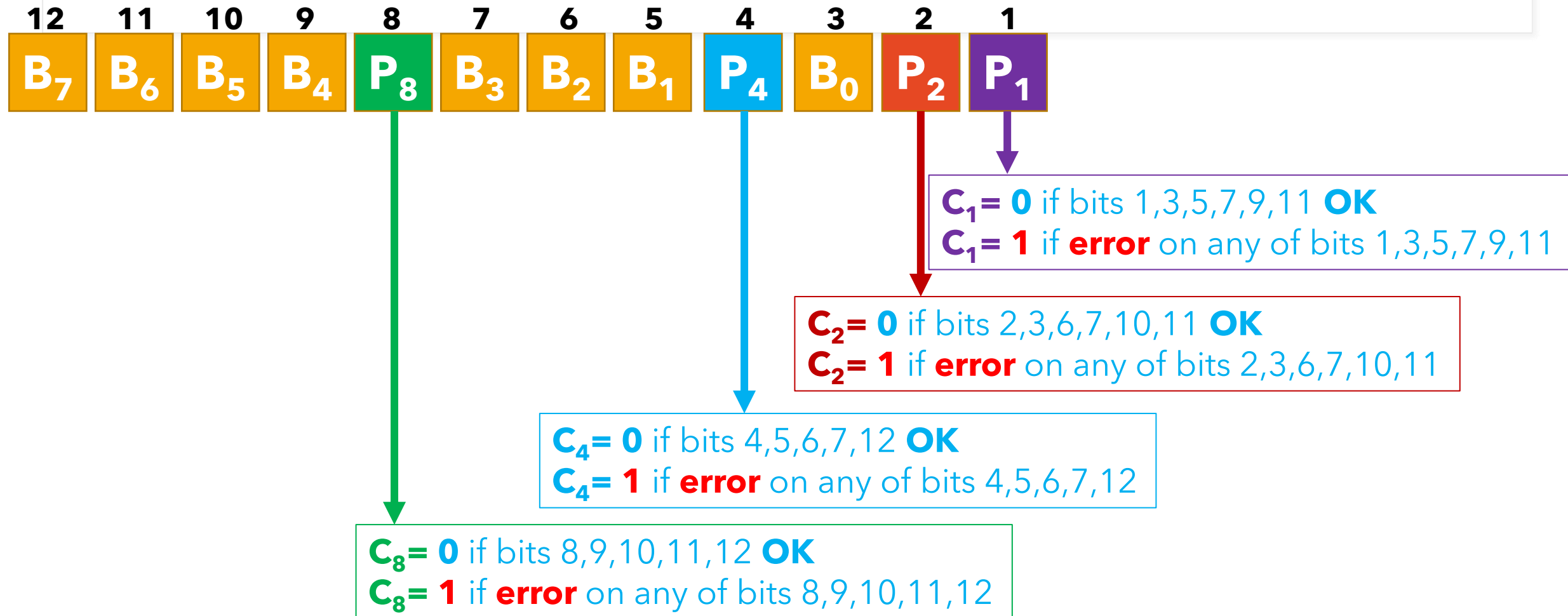

Error Correction with Hamming Codes

				C_1
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0

$C_1 = 0$ if bits 1,3,5,7,9,11 OK

$C_1 = 1$ if error on any of bits 1,3,5,7,9,11

C_1 gives Bit 1 of the erroneous bit position

$C_2 = 0$ if bits 2,3,6,7,10,11 OK

$C_2 = 1$ if error on any of bits 2,3,6,7,10,11

C_2 gives Bit 2 of the erroneous bit position

				C_2
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0

Error Correction with Hamming Codes

	C_4			
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0

$C_4 = 0$ if bits 4,5,6,7,12 **OK**

$C_4 = 1$ if **error** on any of bits 4,5,6,7,12

C_4 gives Bit 3 of the erroneous bit position

$C_8 = 0$ if bits 8,9,10,11,12 **OK**

$C_8 = 1$ if **error** on any of bits 8,9,10,11,12

C_8 gives Bit 4 of the erroneous bit position

$C_8 C_4 C_2 C_1$ together give the position of the erroneous bit!

$C_8 C_4 C_2 C_1 = 0$ means no error

Now we can perform Error Correction
(flip the erroneous bit)

	C_8			
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0



Research Areas

- Effect of 3D stacking
- Effect of newer device technologies (e.g., non-volatile memory)
- Trade-offs: Power/Temperature vs. Performance